



The FSM inputs are *Nickel*, *Dime*, and *Quarter*, indicating which coin was inserted. Assume that exactly one coin is inserted on each cycle. The outputs are *Dispense*, *ReturnNickel*, *ReturnDime*, and *ReturnTwoDimes*. When the FSM reaches 25 cents, it asserts *Dispense* and the necessary *Return* outputs required to deliver the appropriate change. Then, it should be ready to start accepting coins for another soda.

- a. Draw the state transition diagrams that identify the states and any input and outputs to the system
- b. Create a truth table that relates the inputs (including present states of flip-flops, Q0, Q1, etc.) to the next states and outputs of the system
- c. Derive the functional expressions that relate the inputs to the next states and outputs
- d. Build the state machine in JLS (will be a separate Gradescope submission for the JLS file)
- e. Simulate the state machine to insure that it works properly